



## Session **3** Lab Report: **BJT,**

Nooshin Pourkamali, Georgii Molyboga, Julian Clemente Apel

June 2025

## Absolute Maximum Ratings

Stresses exceeding the absolute maximum ratings may damage the device. The device may not function or be operable above the recommended operating conditions and stressing the parts to these levels is not recommended. In addition, extended exposure to stresses above the recommended operating conditions may affect device reliability. The absolute maximum ratings are stress ratings only. Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Value	Unit
$V_{CBO}$	Collector-Base Voltage	BC546	80
		BC547 / BC550	50
		BC548 / BC549	30
$V_{CEO}$	Collector-Emitter Voltage	BC546	65
		BC547 / BC550	45
		BC548 / BC549	30
$V_{EBO}$	Emitter-Base Voltage	BC546 / BC547	6
		BC548 / BC549 / BC550	5
$I_C$	Collector Current (DC)	100	mA
$P_C$	Collector Power Dissipation	500	mW
$T_J$	Junction Temperature	150	$^\circ\text{C}$
$T_{STG}$	Storage Temperature Range	-65 to +150	$^\circ\text{C}$

## Electrical Characteristics

Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Conditions	Min.	Typ.	Max.	Unit
$I_{CBO}$	Collector Cut-Off Current	$V_{CB} = 30\text{ V}, I_E = 0$			15	nA
$h_{FE}$	DC Current Gain	$V_{CE} = 5\text{ V}, I_C = 2\text{ mA}$	110		800	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 0.5\text{ mA}$		90	250	mV
		$I_C = 100\text{ mA}, I_B = 5\text{ mA}$		250	600	
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 0.5\text{ mA}$		700		mV
		$I_C = 100\text{ mA}, I_B = 5\text{ mA}$		900		
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE} = 5\text{ V}, I_C = 2\text{ mA}$	580	660	700	mV
		$V_{CE} = 5\text{ V}, I_C = 10\text{ mA}$			720	
$f_T$	Current Gain Bandwidth Product	$V_{CE} = 5\text{ V}, I_C = 10\text{ mA}, f = 100\text{ MHz}$		300		MHz
$C_{ob}$	Output Capacitance	$V_{CB} = 10\text{ V}, I_E = 0, f = 1\text{ MHz}$		3.5	6.0	pF
$C_{ib}$	Input Capacitance	$V_{EB} = 0.5\text{ V}, I_C = 0, f = 1\text{ MHz}$		9		pF
NF	Noise Figure	BC546 / BC547 / BC548		2.0	10.0	dB
		BC549 / BC550		1.2	4.0	
		BC549		1.4	4.0	
		BC550		1.4	3.0	

## $h_{FE}$ Classification


Classification	A	B	C
$h_{FE}$	110 ~ 220	200 ~ 450	420 ~ 800

# Preparation 1


①  $V_{CE_{max}} = 65V$   $I_{C_{max}} = 100mA$   
 $h_{FE} = 110$   $V_{BE} = 0,66V$  at  $2mA$   
 $(V_{CE} = 5V, I_C = 2mA)$

②  $I_C = 0 \dots 2mA$  DC current gain  $h_{FE(min)} = 110$   
 $I_B = \frac{I_C}{h_{FE(min)}} \Rightarrow$  for  $I_C = 2mA$   $I_B = \frac{2mA}{110} = 18,18 \mu A$   
 $U_{CE} = 0 - 10V$

$U_{CE}, V$	0	6,12	6,09	6,07	6,05	6,04
$I_C, mA$	0	0,5	1	1,5	1,75	2
Calculated $I_B, \mu A$	0	4,54	9,09	13,6	15,9	18,18
Measured $I_B, \mu A$	0	3,43	7	10,6	13,8	14,51

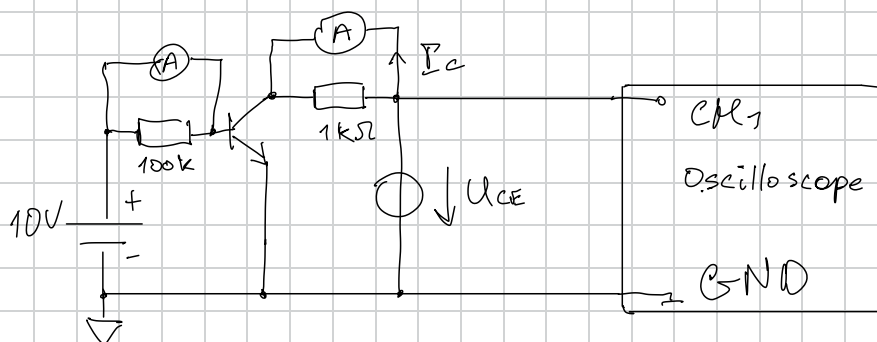

BC546A - Output characteristics (theory)

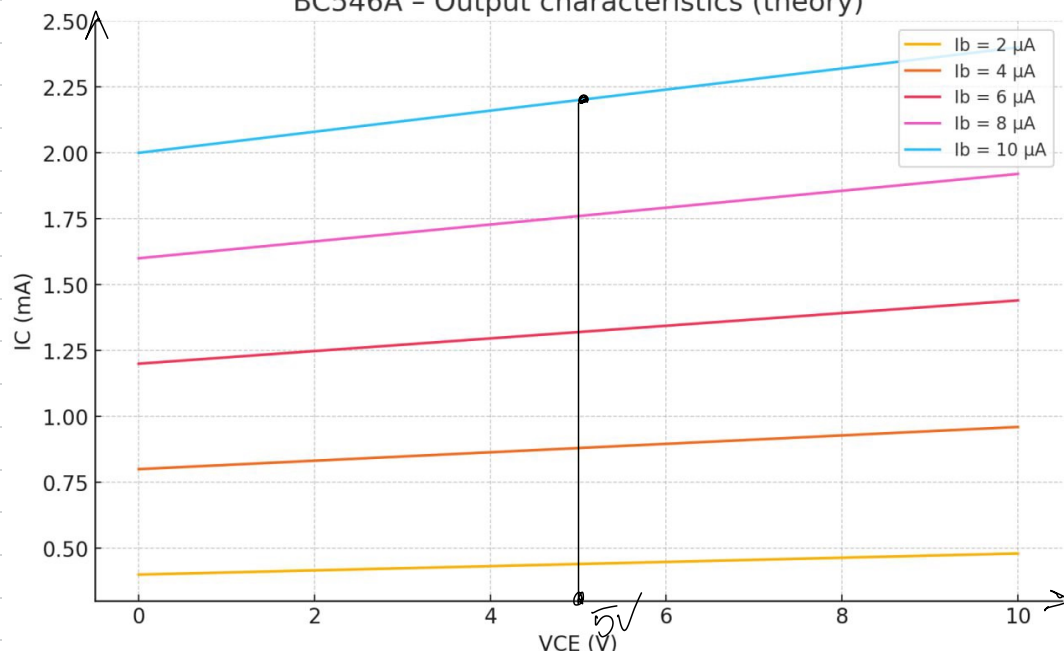


Average current gain

$I_{gain} \approx 2,2 mA$

Early voltage

$V_A \approx 50V$

## Preparation 2

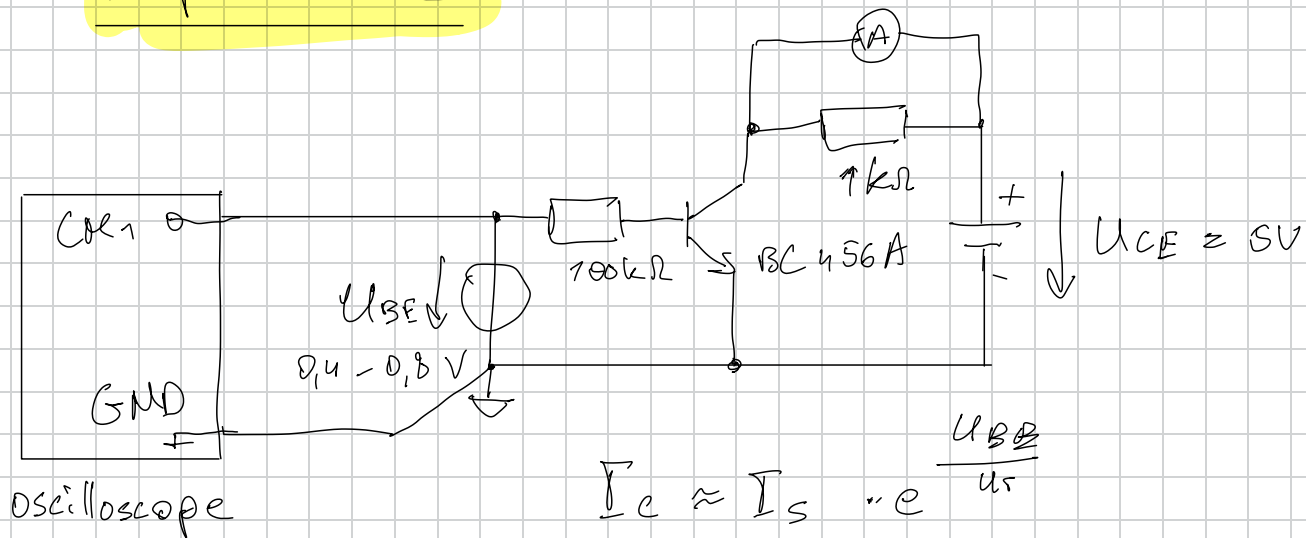

$$I_S \approx 1 \cdot 10^{-14} \text{ A typically}$$

$U_T \approx 25 \text{ mV}$  at room temperature

Approximate values:

$U_{BE}, \text{mV}$	500	600	650	700	720	740	750
Calculated $I_C$	$1.9 \mu\text{A}$	$110 \mu\text{A}$	$820 \mu\text{A}$	$6.1 \text{mA}$	$1.7 \text{mA}$	$4.6 \mu\text{A}$	$7.4 \mu\text{A}$
Measured $I_C$	$60 \mu\text{A}$	$147 \mu\text{A}$	$198 \mu\text{A}$	$250 \mu\text{A}$	$270 \mu\text{A}$	$296 \mu\text{A}$	$307 \mu\text{A}$


## Evaluation 2

Transconductance at  $I_C = 1 \text{ mA}$

$$I_S = I_C \cdot e^{-\frac{U_{BE}}{U_T}}$$

$$g_m = 40 \text{ mS}$$

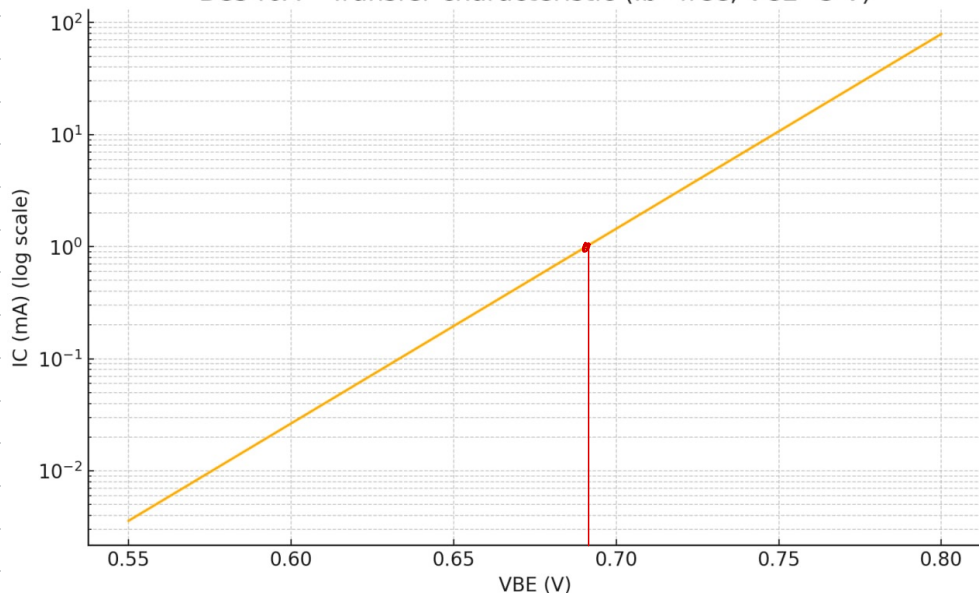BC546A - Transfer characteristic ( $I_b = \text{free}$ ,  $V_{CE} = 5 \text{ V}$ )



$I_S \approx 1 \cdot 10^{-15} \text{ A}$   
Saturation  
current

### Preparation 3.

Assuming  $U_B = 10V$

Let's say  $U_{CE} = \frac{1}{2} U_B = 5V$

$$R_C = \frac{U_B - U_{CE}}{I_C} = \frac{10V - 5V}{2mA} = 2,5 k\Omega$$

(collector resistor)

$\downarrow$   
 $2,7 k\Omega$  (E12)

$U_E \approx 10\% \text{ of } U_B = 1V$

$$R_E = \frac{U_E}{I_E} = 500\Omega \rightarrow \underline{560\Omega \text{ (E12)}}$$

(emitter resistor)


$$V_B = U_E + U_{BE} \approx 1V + 0,65V = 1,65V$$

Divider Current  $\approx 10 \cdot I_B \approx 0,18 mA$


$$R_2 = \frac{V_B}{0,18mA} = \underline{9,16 k\Omega} \Rightarrow (8,2 + 1) k\Omega$$

$$R_1 = \frac{U_B - V_B}{0,18 mA} = \underline{46,39 k\Omega} \Rightarrow (4,7 \cdot 10) k\Omega$$

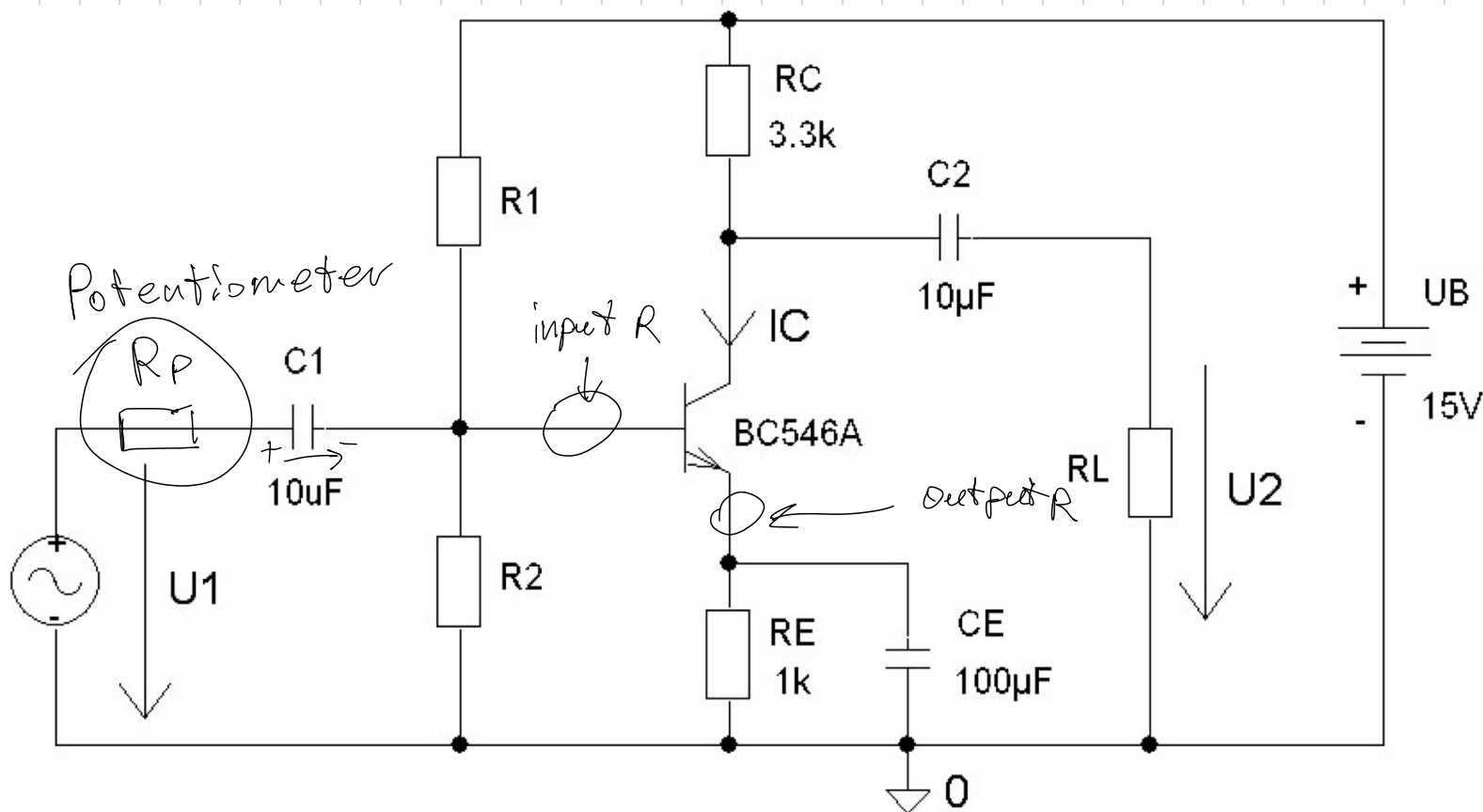
in practice  $R_2 \sim 10k\Omega$  and  $R_1 \sim 100k\Omega$



# Results from the LAB

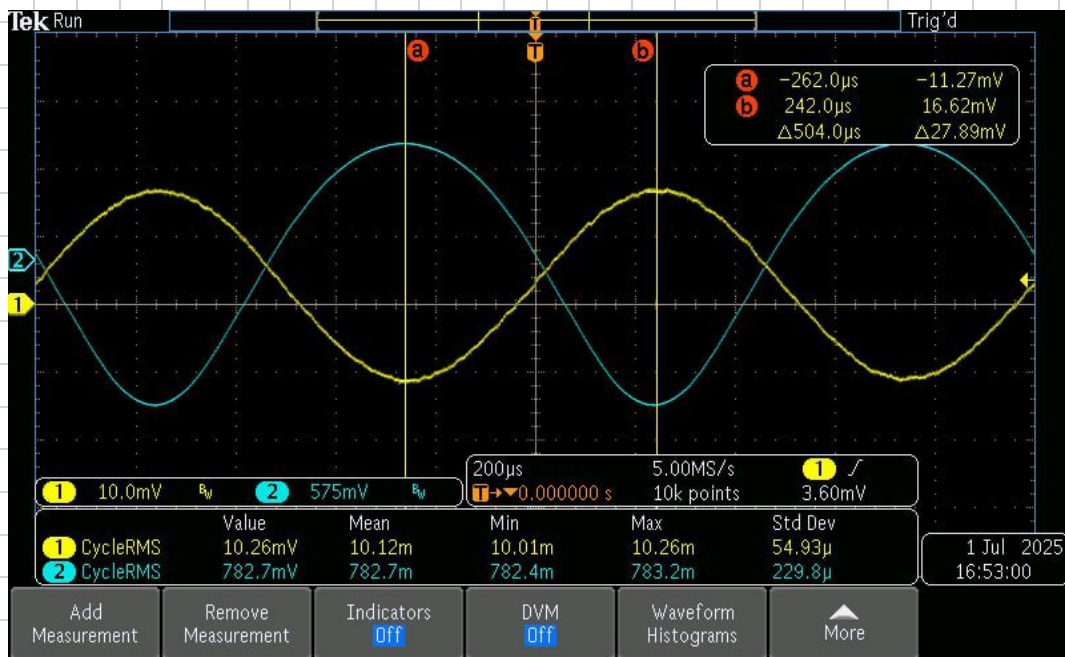

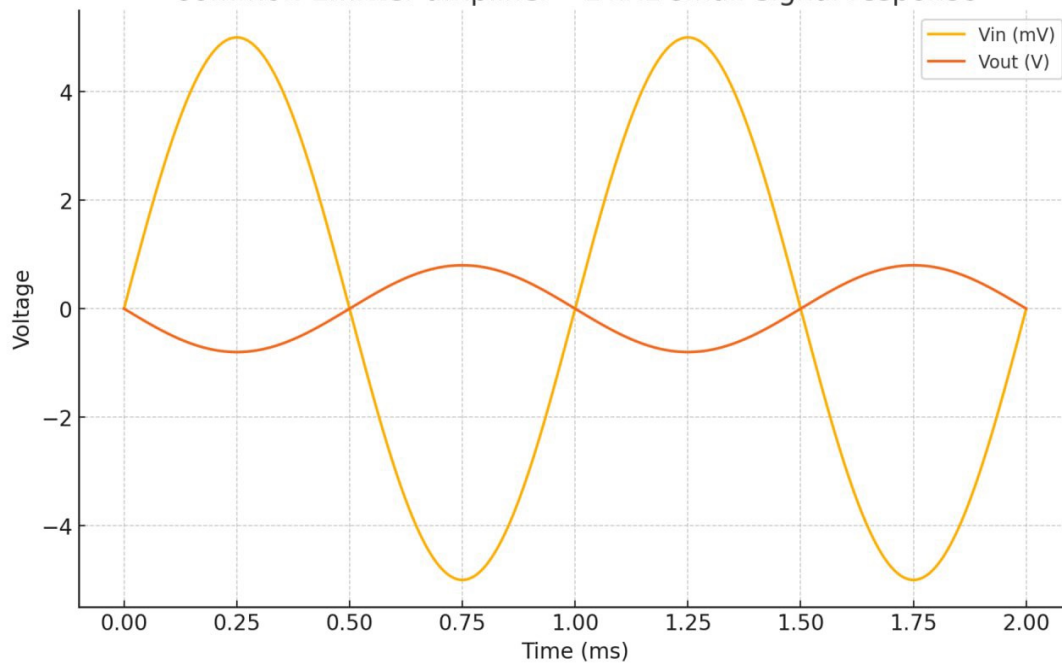Common-Emitter amplifier - 1 kHz small-signal response



Measured internal resistance  $R_{in} = 830 \Omega$   
 output resistance  $R_{out} = 2,9 k\Omega$